

- Generates a high-frequency signal to switch power transistors.
- Often implemented using ICs or oscillators like the 555 timer or microcontrollers.

2. Power Switching Devices

- Usually MOSFETs or IGBTs capable of handling high currents and voltages.
- Switch on and off rapidly to create the AC waveform.

3. Transformer

- Steps up the low-voltage DC to the desired AC voltage.
- Provides isolation and voltage transformation.

4. Filter and Waveform Shaping Circuit

- Ensures the output waveform is a pure sinewave.
- Uses filters like LC (Inductor-Capacitor) filters or more advanced circuits like PWM (Pulse Width Modulation).

5. Feedback and Control Circuit

- Monitors the output waveform.
- Adjusts the switching signals to maintain a pure sinewave.

6. Protection Circuits


- Overload protection, short circuit protection, and thermal shutdown.

Basic Circuit Diagram of a 1000W Sinewave Inverter

Below is a simplified overview of the circuit components involved:

``plaintext

DC Power Source (Battery)

 

Oscillator Control Circuit Protection Circuit



Gate Drive Feedback Loop |



MOSFETs/IGBTs (Switching Devices)



Transformer (Step-up)



LC Filter (Waveform Smoothing)



AC Output (Pure Sinewave)



This block diagram provides a high-level view; actual circuitry involves detailed connections and component specifications.

Detailed Circuit Diagram of a 1000W Sinewave Inverter

A typical 1000W sinewave inverter circuit can be divided into the following sections:

1. Oscillator and PWM Generator

- Usually built using a dedicated IC like SG3525 or a microcontroller.

